
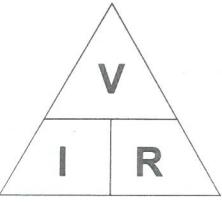
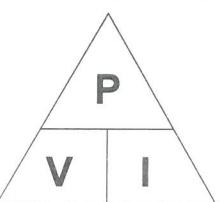
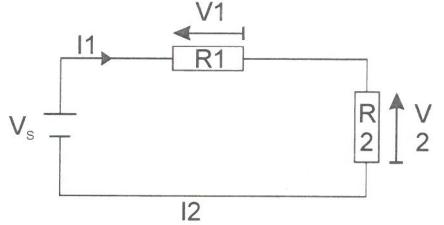


Equations for C&G 2365 Level 2

<h2>Ohm's Law</h2>	 <p>Where: V = Voltage (Volts (V)) I = Current (Amps (A)) R = Resistance (Ohms (Ω)))</p>	$R = V / I$ $I = V / R$ $V = I \times R$ $17.69\Omega = 230V / 13A$ $13A = 230V / 17.69\Omega$ $230V = 13A \times 17.69\Omega$
<h2>Power</h2>	 <p>Where: P = Power (Watts (W)) V = Voltage (Volts (V)) I = Current (Amps (A))</p>	$P = V \times I$ $V = P / I$ $I = P / V$ $3kW = 230V \times 13A$ $230V = 3kW / 13A$ $13A = 3kW / 230V$
	<p>Combined with Ohm's Law:</p> $P = I^2 R$ $P = V^2 / R$	$3kW = 13A^2 \times 17.69\Omega$ $3kW = 230V^2 / 17.69\Omega$
<h2>Series Circuits</h2>	 <p>V_s = Voltage at Source $V_s = V1 + V2$ $I = I1 = I2$ (current remains same throughout circuit) $V1 = R1 \times I$ $R2 = V2 / I$ $I = V1 / R1$ $R_{TOT} = R1 + R2$</p>	$230V (V_s) = 110V (V1) + 120V (V2)$ $I = 13A$ $110V (V1) = 8.46\Omega (R1) \times 13A$ $9.23\Omega (R2) = 120 / 13A$ $13A = 110 / 8.46\Omega$ $R_{TOT} = 8.46 + 9.23 = 17.69\Omega$

Equations for C&G 2365 Level 2

Parallel Circuits

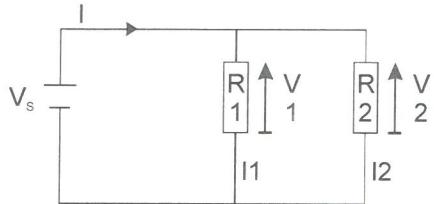

$V_s = V_1 = V_2$
(voltage remains same throughout circuit)

$$I = I_1 + I_2$$

$$I_1 = V_1 / R_1$$

$$V_2 = I_2 \times R_2$$

$$R_2 = V_2 / I_2$$

$$R_{\text{TOT}} = \frac{R_1 \times R_2}{R_1 + R_2} \quad (\text{Only usable for 2 loads})$$

$$\frac{1}{R_{\text{TOT}}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (\text{Usable for multiple loads})$$

$$V_s = 230V$$

$$I_1 = 230V / 12\Omega (R_1) = 19.167A$$

$$R_2 = 230V / 16A (I_2) = 14.375\Omega$$

$$R_{\text{TOT}} = \frac{12\Omega \times 14.375\Omega}{12\Omega + 14.375\Omega} = 6.54\Omega$$

$$I = 19.167 + 16 = 35.167A$$

$$\begin{aligned} \frac{1}{R_{\text{TOT}}} &= \frac{1}{12\Omega} + \frac{1}{14.375\Omega} \\ &= \frac{1.198}{14.375\Omega} + \frac{1}{14.375\Omega} \\ &= \frac{2.198}{14.375\Omega} \end{aligned}$$

$$\therefore R_{\text{TOT}} = \frac{14.375}{2.198} = 6.54\Omega$$

Resistance in length of cable

$$R = \frac{\rho l}{A}$$

Where:

ρ = Specific resistivity of material (Ωm)

l = Length of material (m)

A = Cross-sectional area of material (m^2)

$$1mm^2 = 1 \times 10^{-6}m^2$$

Specific resistivities:

Silver = 16.4×10^{-9}

Copper = 17.5×10^{-9}

Aluminium = 28.5×10^{-9}

Brass = 75.0×10^{-9}

Iron = 100.0×10^{-9}

Stainless Steel 690×10^{-9}

Resistance of 10m of $2.5mm^2$ Copper cable:

$$R = \frac{17.5 \times 10^{-9} \times 10}{2.5 \times 10^{-6}}$$

$$R = \frac{17.5 \times 10^{-3} \times 10}{2.5}$$

$$R = \frac{0.0175 \times 10}{2.5}$$



$$R = \frac{0.175}{2.5}$$

$$R = 0.07\Omega$$

$$R \propto l \quad \alpha = \text{proportional}$$


$$R \propto \frac{1}{A}$$

Equations for C&G 2365 Level 2

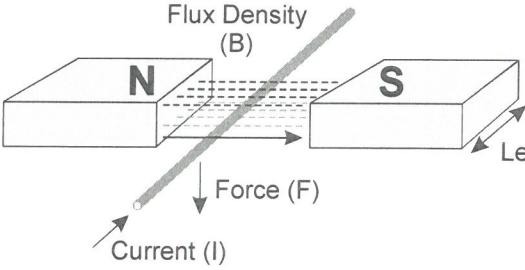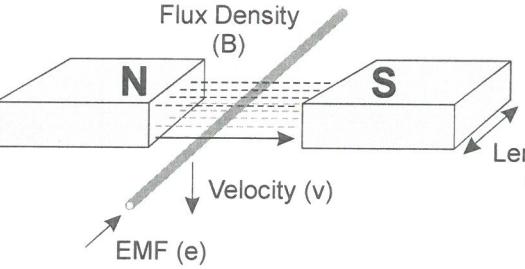
Frequency	$F = \frac{1}{T}$ Where: F = Frequency (Hz) T = Time of single cycle (s)	$50\text{Hz} = \frac{1}{0.02\text{s}}$
Motor Action	 <p>A diagram illustrating the motor effect. A rectangular conductor is shown moving to the right through a uniform magnetic field represented by dashed lines between two permanent magnets, one labeled 'N' (North) and one labeled 'S' (South). The conductor has an arrow indicating its direction of motion. The magnetic field is labeled 'Flux Density (B)'. The length of the conductor within the field is labeled 'Length of conductor within field (L)'. A downward-pointing arrow on the conductor is labeled 'Current (I)'. A horizontal arrow pointing to the right from the conductor is labeled 'Force (F)'.</p> $F = B I L$ <p>Where: F = Force (N) B = Flux Density (Tesla (T)) I = Current (A) L = Length of conductor (m)</p>	
Generator Action	 <p>A diagram illustrating the generator effect. A rectangular conductor is shown moving to the right through a uniform magnetic field represented by dashed lines between two permanent magnets, one labeled 'N' (North) and one labeled 'S' (South). The conductor has an arrow indicating its direction of motion. The magnetic field is labeled 'Flux Density (B)'. The length of the conductor within the field is labeled 'Length of conductor within field (L)'. A downward-pointing arrow on the conductor is labeled 'Velocity (v)'. An upward-pointing arrow at the end of the conductor is labeled 'EMF (e)'.</p> $e = B L v$ <p>Where: e = EMF (V) B = Flux Density (Tesla (T)) L = Length of conductor (m) v = Velocity (m/s)</p>	

Equations for C&G 2365 Level 2


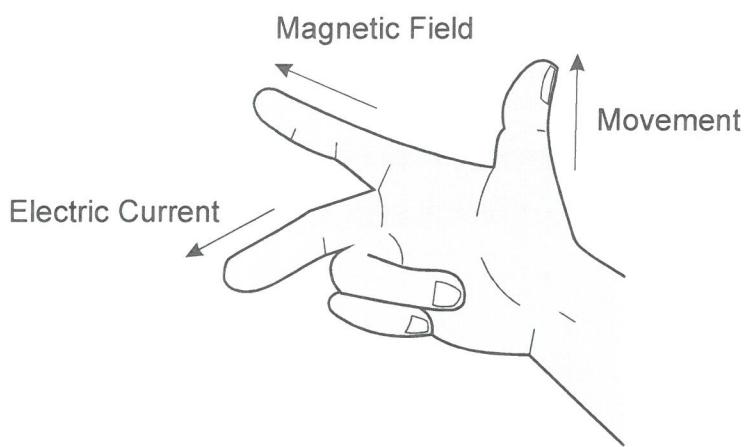
**Flemming's
Right Hand
Rule
(Generator)**



**Flemming's
Left Hand
Rule
(Motor)**

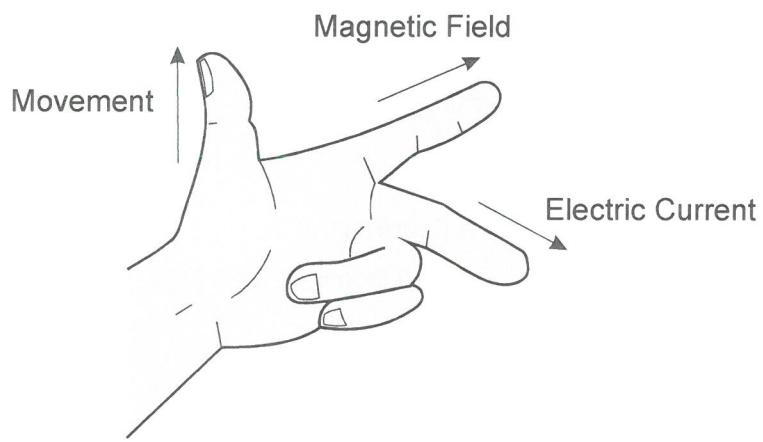


**Flemming's
Right Hand
Grip Rule**

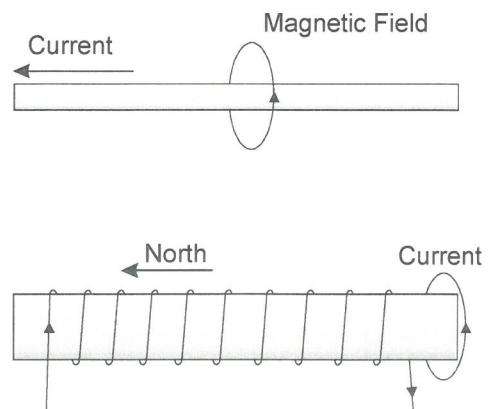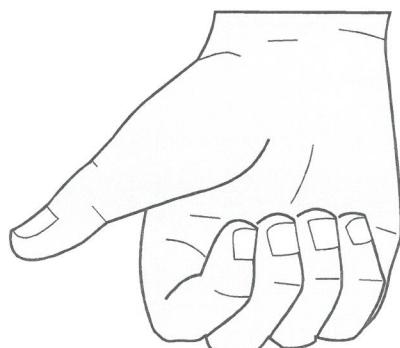

Equations for C&G 2365 Level 2

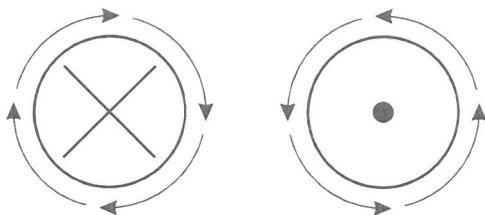
Direction of magnetic fields produced by cables



\times = Current flowing away (dart flights)

\bullet = Current flowing towards (dart point)

AC Sine Wave

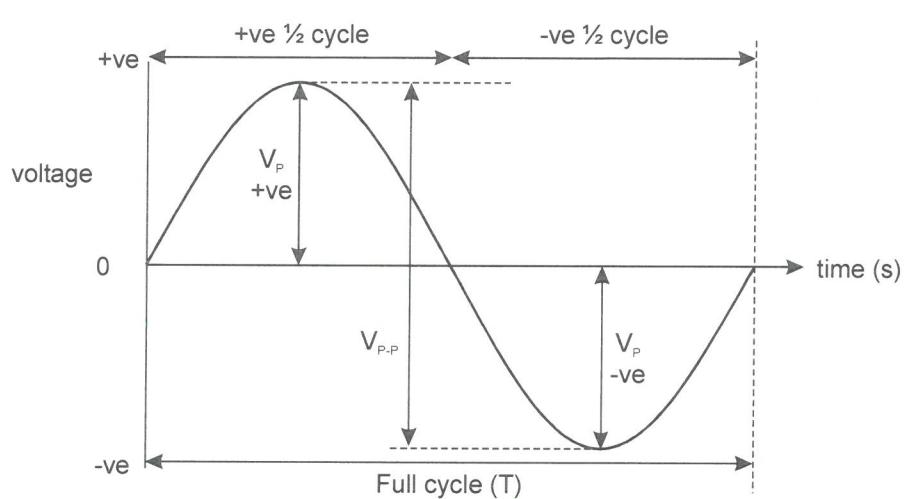

V_p = Voltage Peak

$T = 20\text{ms}$

$V_{p.p} = \text{Voltage Peak to Peak}$

$$230V = \frac{325V}{\sqrt{2}}$$

$$V_{RMS} = \frac{V_p}{\sqrt{2}}$$


$$50\text{Hz} = \frac{1}{20 \times 10^{-3}}$$

$$1\text{ms} = 1 \times 10^{-3}\text{s}$$

$$F(\text{Hz}) = \frac{1}{T(\text{s})}$$

Equations for C&G 2365 Level 2


AC Power Generation (Alternator)

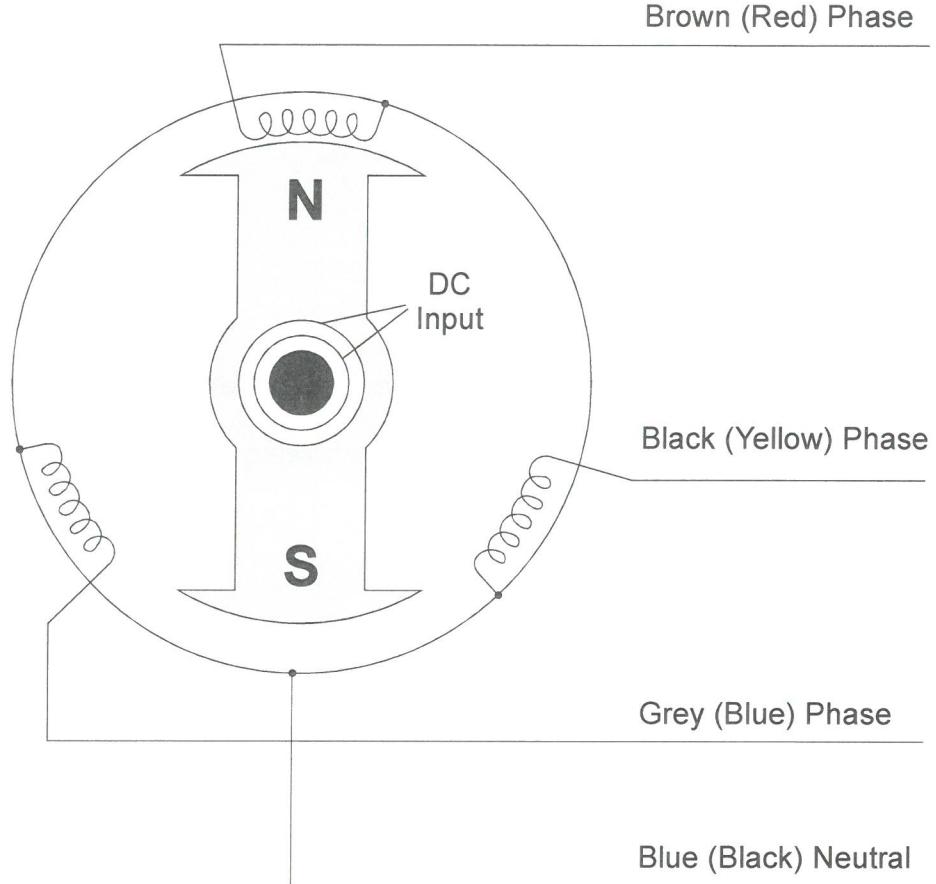


Windings are evenly spaced at 120°

DC electro magnet in centre

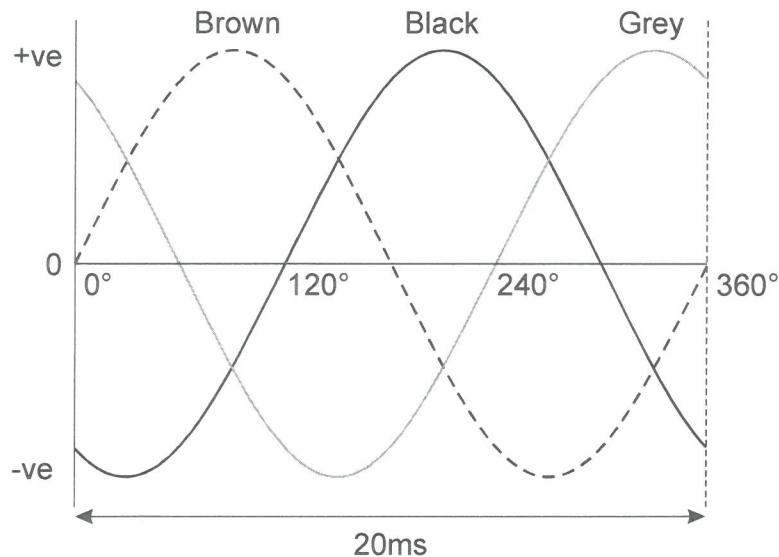Generator speed = $50\text{Hz} \times 60 \text{ seconds} = 3000\text{RPM}$




Equations for C&G 2365 Level 2
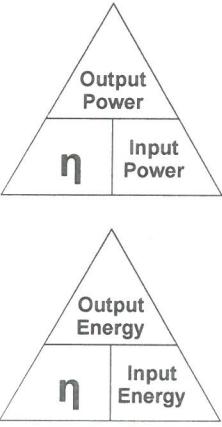
<h2>Mechanical Calculations</h2>	<p>$F = m a$</p> <p>Where:</p> <p>F = Force (Newtons (N)) m = mass (kg) a = acceleration (ms^{-2})</p> <p>Gravitational acceleration $= 9.81\text{ms}^{-2}$</p>	$981\text{N} = 100\text{kg} \times 9.81\text{ms}^{-2}$
	<p>$W_d = F D$</p> <p>Where:</p> <p>W_d = Work done (Nm) F = Force (N) D = Distance (m)</p> <p>$1\text{Nm} = 1\text{ Joule(J)}$</p>	$9810\text{J} = 9810\text{Nm} = 981\text{N} \times 10\text{m}$
	<p>$P = \frac{W_d}{t}$</p> <p>Where:</p> <p>P = Power (W) W_d = Work done (J) t = Time (s)</p> <p>$1\text{W} = 1\text{ Joule per second (Js)}$</p>	$16.35\text{W} = \frac{9810\text{J}}{600\text{s}}$
<h2>Efficiency</h2>	 <p>Where: η = Efficiency (as ratio)</p> <p>Efficiency as % = Efficiency ratio $\times 100$</p>	$\eta = \frac{9810\text{W}}{14010\text{W}} = 0.7$

Equations for C&G 2365 Level 2

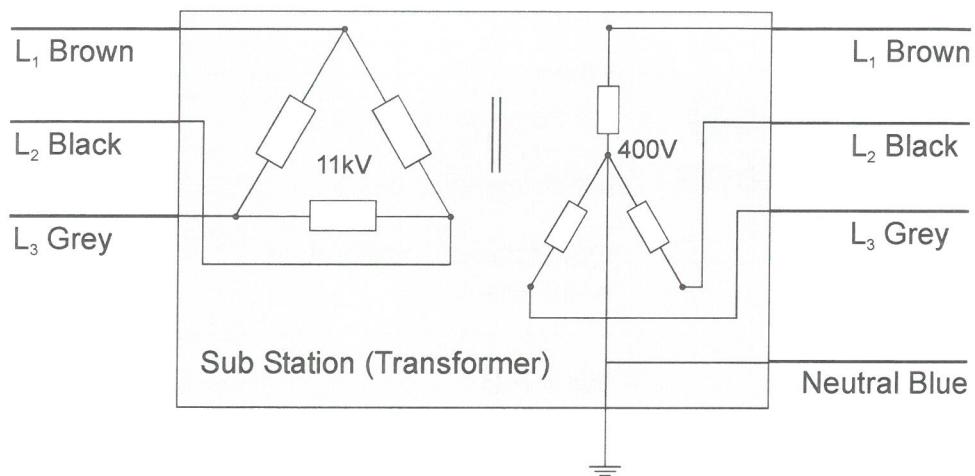230V Single Phase & 400V 3 Phase Supplies




Input Line to line on the input side will give you 11kV

Output Line to line (or Phase to Phase) on the output side will give you 400V
Any line to neutral will give you 230V

Domestic supplies will use one phase to neutral at 230V, protected by a 100A fuse.

Delta-Star (or Delta-Wye) Transformer

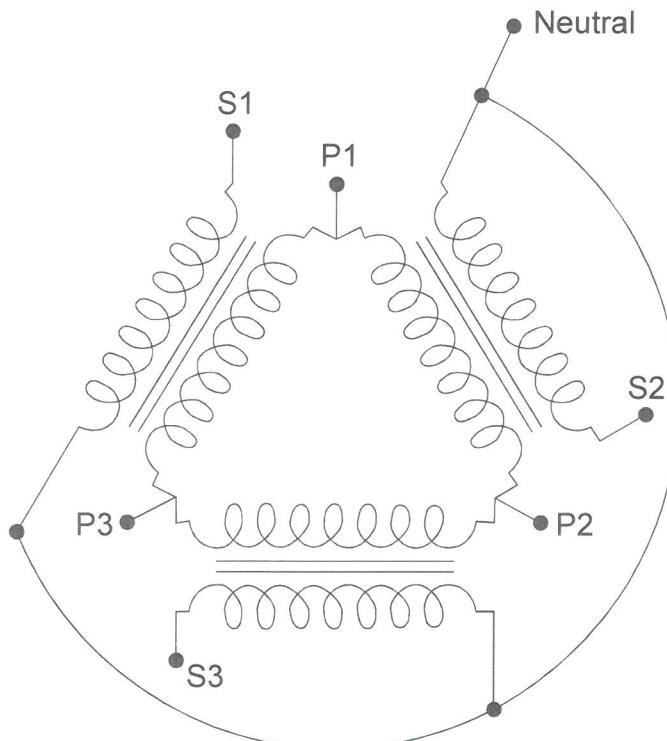


Equations for C&G 2365 Level 2


UK Power Generation & Distribution Voltages	Voltage	Description
	25kV	Generation Electricity is generated as 25kV as we do not have a useful insulator beyond that voltage.
	275kV or 400kV	National Grid & Super Grid Used for long distance distribution
	132kV	Supply to local distribution companies
	33kV	Regional distribution & heavy industry
	11kV	Towns, villages & small industry
	400V	Commercial
	230V Single phase	Domestic & Commercial

Equations for C&G 2365 Level 2


Star 3 Phase Circuits

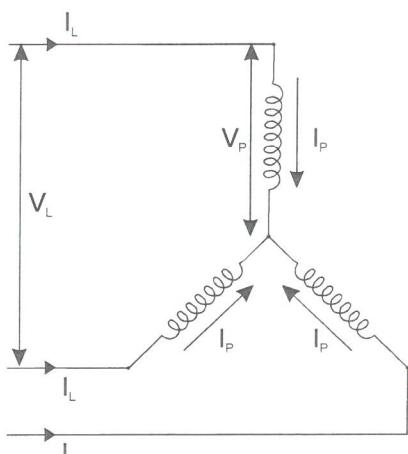


$$400V = \sqrt{3} \times 230V$$

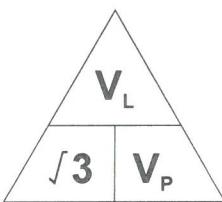

Delta 3 Phase Circuits

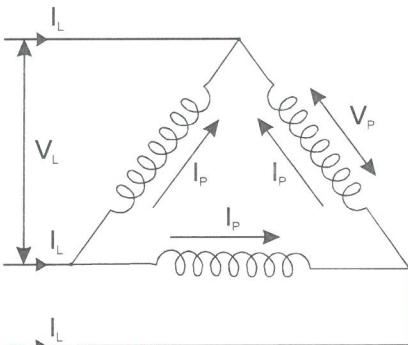

$$22.6A = \sqrt{3} \times 13A$$

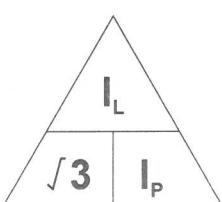

Power (3 Phase Circuits)

Balanced Load(Ω)

$$\text{Power (W)} = \sqrt{3} \times V_L \times I_L \times \cos \Phi$$


Where: V_L = Line Voltage (V)
 I_L = Line Current (A)
 $\cos \Phi$ = Power Factor (p.f.)

Load(Ω) in each phase must be identical otherwise power for each phase must be calculated individually.

$$P_{\text{TOT}} = \sqrt{3} \times 400 \times 23 \times 0.7$$


$$P_{\text{TOT}} = 11.2kW$$

Equations for C&G 2365 Level 2
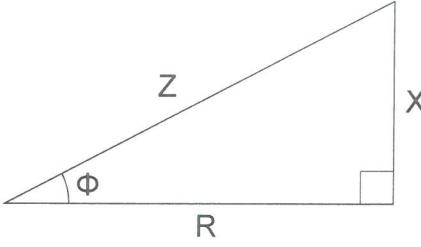
<h2>Impedance Triangle</h2>	 <p>Where: X = Reactance (Ω) R = Resistance (Ω) Z = Impedance (Ω) $\cos \Phi$ = Power Factor (p.f.)</p> <p>From Pythagoras:</p> $Z = \sqrt{R^2 + X^2} \quad \Omega$ <p>From Trigonometry:</p> $\cos \Phi = \frac{R}{Z}$ $X = \left X_C - X_L \right \quad (\text{Modulus meaning difference between})$	$X = \left 10 - 12 \right = 2\Omega$ $Z = \sqrt{15^2 + 2^2} \quad \Omega = 15.133\Omega$ $\cos \Phi = \frac{15}{15.133} = 0.99$
<h2>Inductive Reactance (X_L)</h2>	$X_L = 2\pi fL \quad \Omega$ <p>Where: f = Frequency (Hz) L = Inductance (Henrys)</p>	$L = 50mH = 50 \times 10^{-3} = 0.05H$ $X_L = 2 \times \pi \times 50Hz \times 0.05H \quad \Omega$ $X_L = 15.708\Omega$
<h2>Capacitive Reactance (X_C)</h2>	$X_C = \frac{1}{2\pi fC} \quad \Omega$ <p>Where: f = Frequency (Hz) C = Capacitance (Farads (F))</p>	$C = 50\mu F = 50 \times 10^{-6} = 0.00005F$ $X_C = \frac{1}{2 \times \pi \times 50Hz \times 0.00005F}$ $X_C = 63.662\Omega$

Equations for C&G 2365 Level 2

Power Triangle

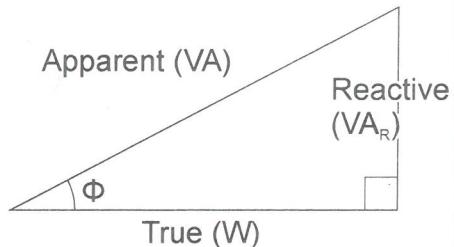

Apparent = Source Power
True = Useful Power
Reactive = Waste Power

$$VA_R = \sqrt{VA^2 - W^2} \Omega$$

$$\cos \Phi = \frac{W}{VA}$$

CIVIL

C	Capacitive Reactance
I	Current
V	Voltage
I	Current
L	Inductive Reactance

Capacitive Reactance
I leads V (CIV)

Inductive Reactance
I lags V (VIL)