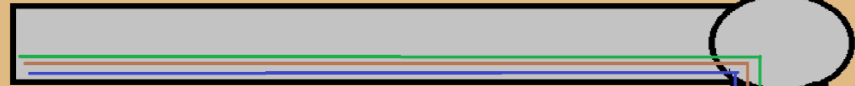


DateCreated: 4/1/2026



IWA

Three plate method - One way switch - one gang

Consumer unit



Angle box

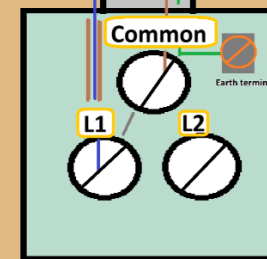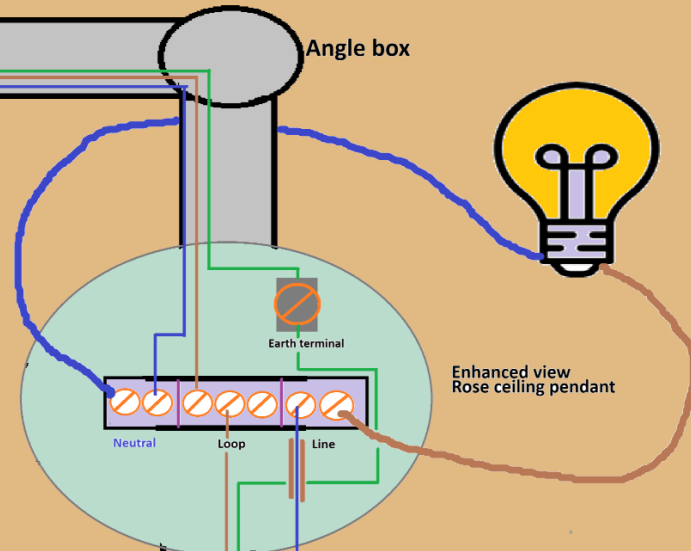

Light switch one

DateCreated: 4/1/2026


IWA

Three plate method - Two way switch


Consumer unit



Angle box

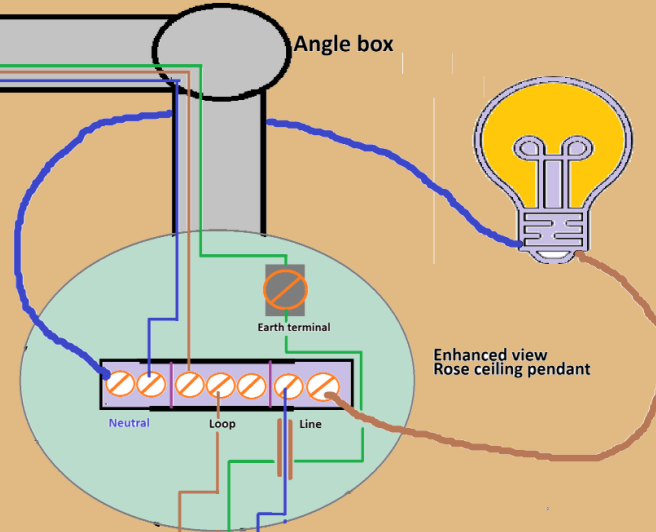

Enhanced view
Rose ceiling pendant

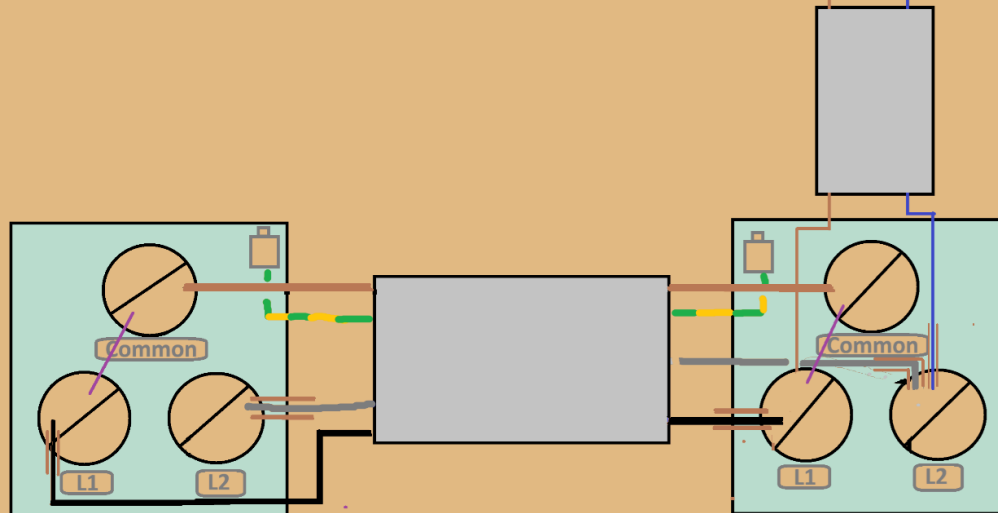

To change a **three plate method one-way switch** to a **three plate method two-way switch**

Ceiling cable

The ceiling cable's **brown live wire** which was in the **common terminal** moves to either the **L1** or **L2 terminal**.

Typically, the **brown live wire** goes into the **L2 terminal** because the **switch-live** wire is typically in the **L1 terminal**.

However, this could not be the case. For example, the **switch-live** wire could be in the **L2 terminal**. In which case the **brown live wire** goes into the **L1 terminal**.

Strapper cable/ 3 core cable

The three core cable consists of a black wire, **brown wire**, grey wire and **cpc wire**.

The strapper cable connects the two light switches together.

The **brown live wire** of the strapper cable goes into the **common terminal**. Conveniently, it occupies the place where the ceiling cable's **brown live wire** used to be.

Either the grey or black wire can go into the **L1 terminal**.

Either the grey or black wire can go into the **L2 terminal**.

The **Brown live wire** always goes into the **common terminal** .