

Sunday 25th of January
IWA

This is an example of how a dimmer switch is implemented. In the above diagram the dimmer switch is implemented using the two plate method. However, we could use a three plate method. The light switch uses electronics in order to facilitate the dimmer effect. The dimmer switch only requires a live brown wire. Therefore, how do we test a dimmer switch?

