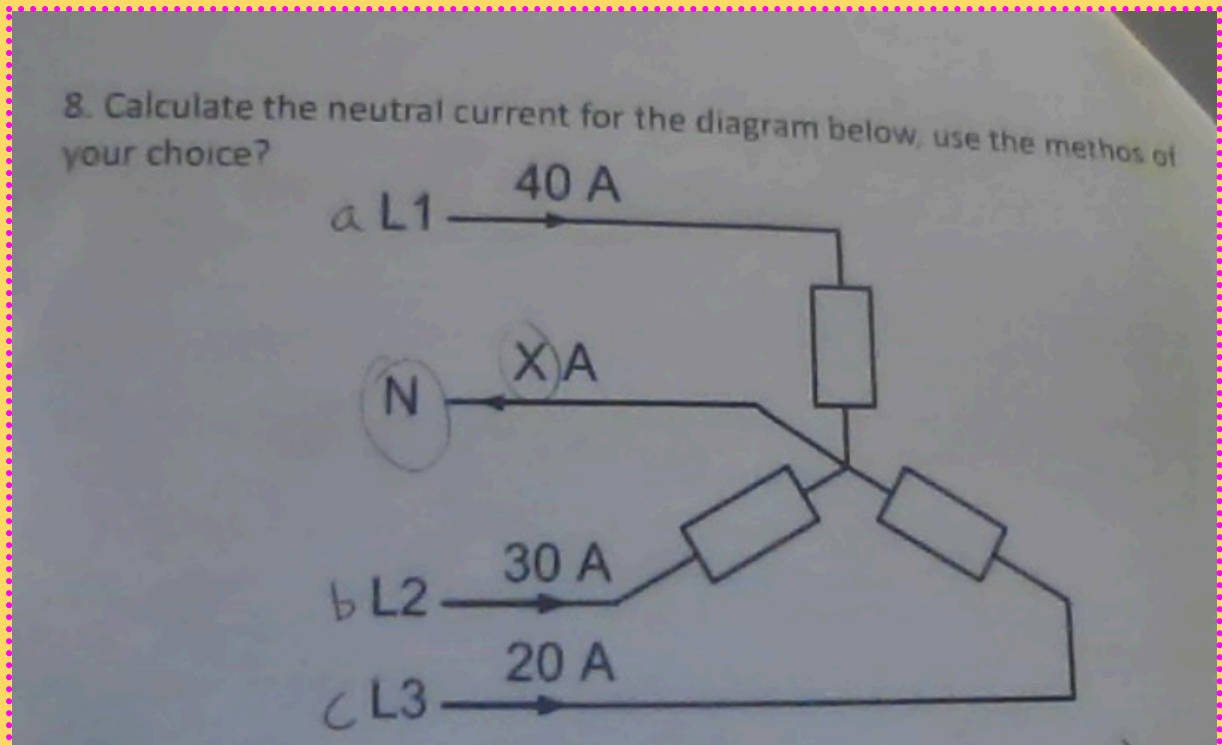


Unit 302 Mock exam

Question 8: Calculate the neutral current for the diagram below, use the methods of your choice?



$$N = \sqrt{((I_a^2 + I_b^2 + I_c^2) - (I_a \times I_b) - (I_b \times I_c) - (I_a \times I_c))}$$
$$N = \sqrt{((40^2 + 30^2 + 20^2) - (40 \times 30) - (30 \times 20) - (40 \times 20))}$$
$$N = \sqrt{(1,600 + 900 + 400) - (1,200) - (600) - (800)}$$
$$N = \sqrt{(2,900) - 1,200 - 600 - 800}$$
$$N = \sqrt{300} = 17.32$$