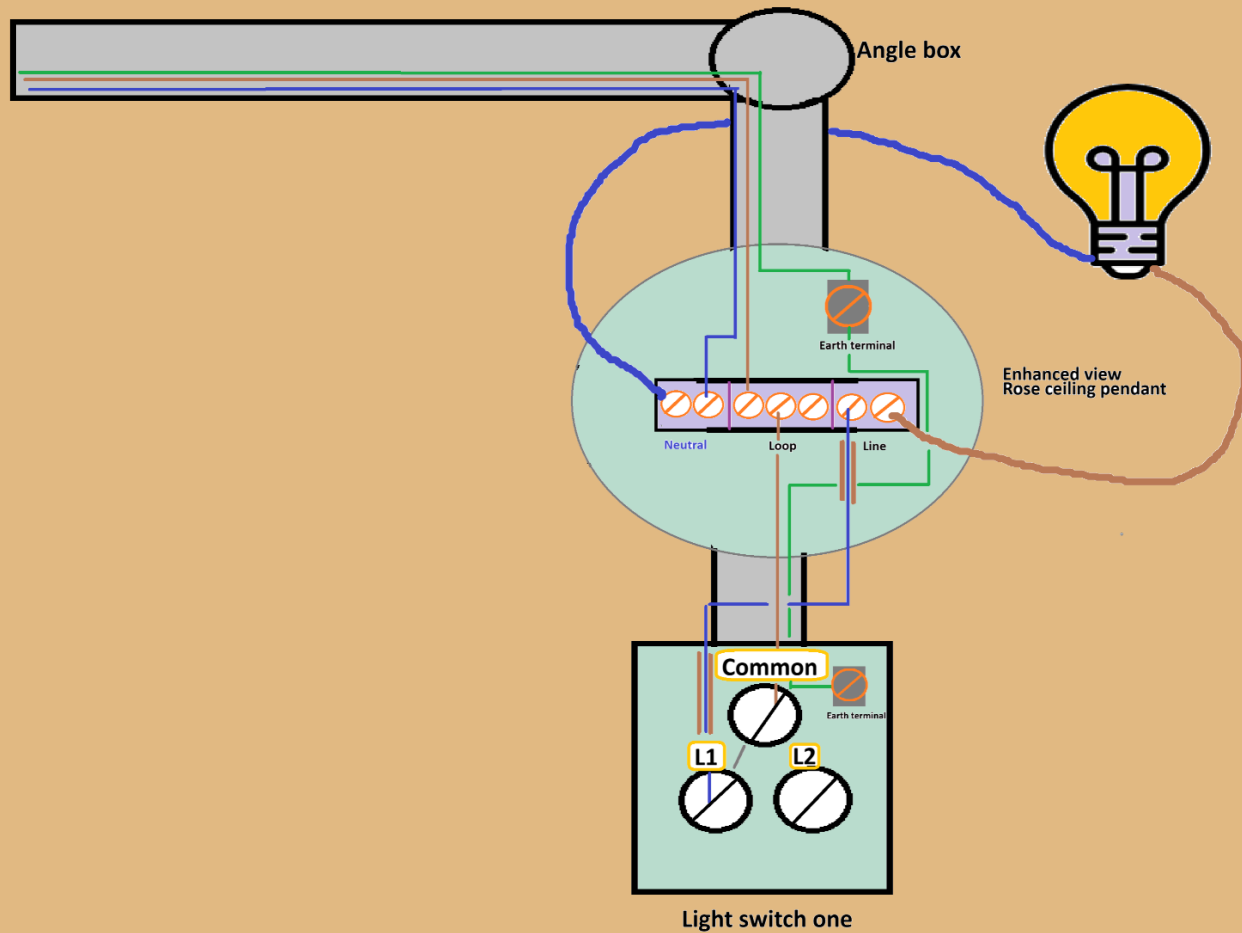


DateCreated: 4/1/2026

IWA

Three plate method - One way switch - one gang

Consumer unit




Three plate method - Two way switch


Consumer unit



Angle box

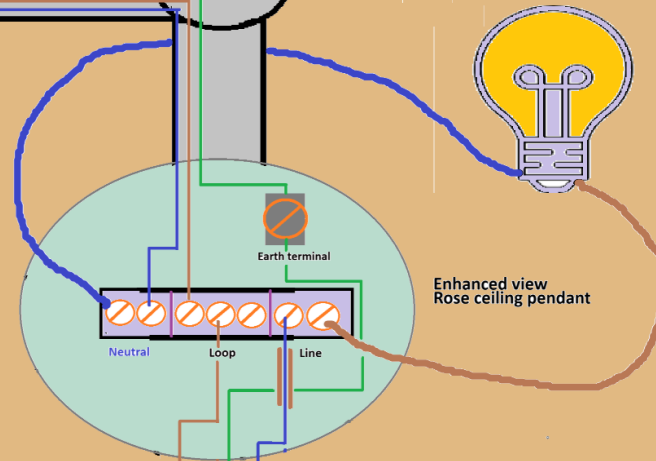

Enhanced view
Rose ceiling pendant

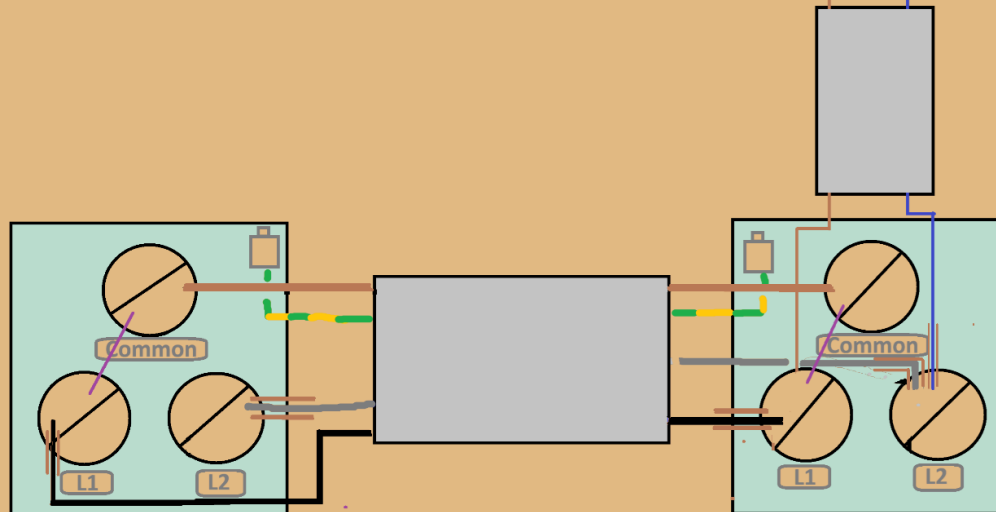

DateCreated: 4/1/2026

IWA

To change a **three plate method one-way switch** to a **three plate method two-way switch**

Ceiling cable

The ceiling cable's **brown live wire** which was in the **common terminal** moves to either the **L1** or **L2 terminal**.

Typically, the **brown live wire** goes into the **L2 terminal** because the **switch-live** wire is typically in the **L1 terminal**.

However, this could not be the case. For example, the **switch-live** wire could be in the **L2 terminal**. In which case the **brown live wire** goes into the **L1 terminal**.

Strapper cable/ 3 core cable

The three core cable consists of a black wire, **brown wire**, **grey wire** and **cpc wire**.

The strapper cable connects the two light switches together.

The **brown live wire** of the strapper cable goes into the **common terminal**. Conveniently, it occupies the place where the ceiling cable's **brown live wire** used to be.

Either the grey or black wire can go into the **L1 terminal**.

Either the grey or black wire can go into the **L2 terminal**.

The **Brown live wire** always goes into the **common terminal**.

Notes


The wires colours are not mandatory rather preferential. Because, the wires are all live so they should be brown.

Upside down Window wiper

DateCreated: 4/1/2026

IWA

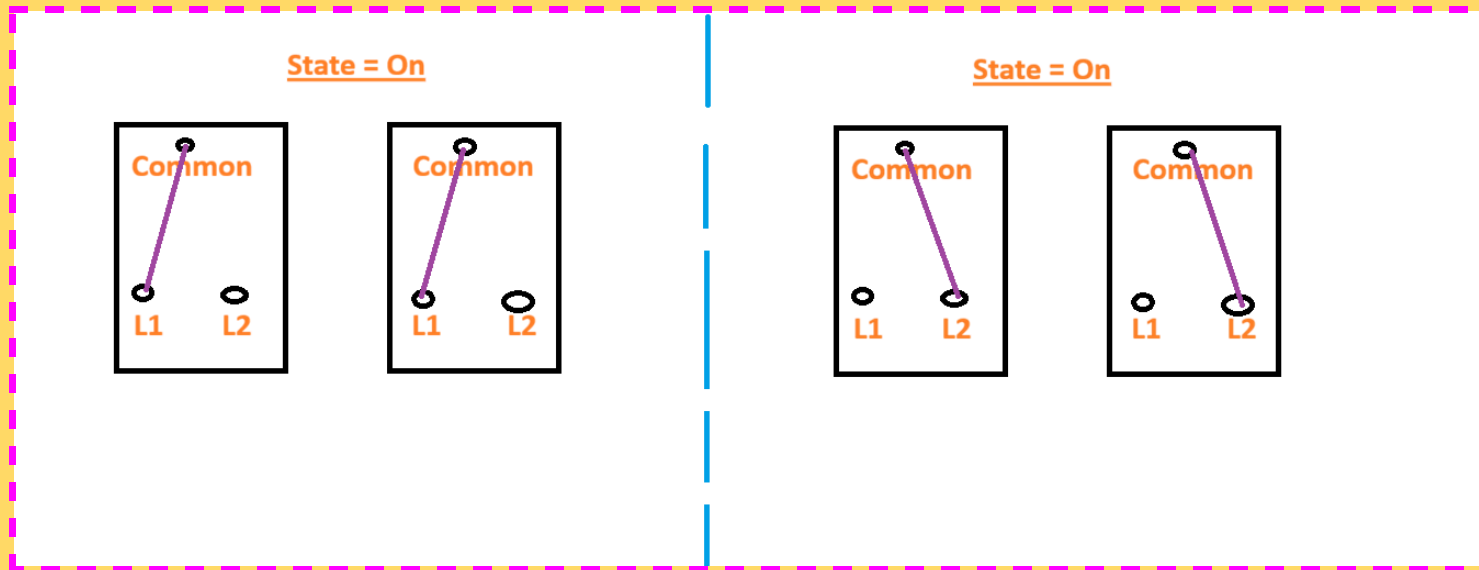The common terminals act like a pendulum and swing back and forth as the end user presses the gang switch. Remember there are four possible states for the light switch. Two of those switches will mean that the light bulb will be on.



The way that the two states are resemble an upside window wiper featured on a car.