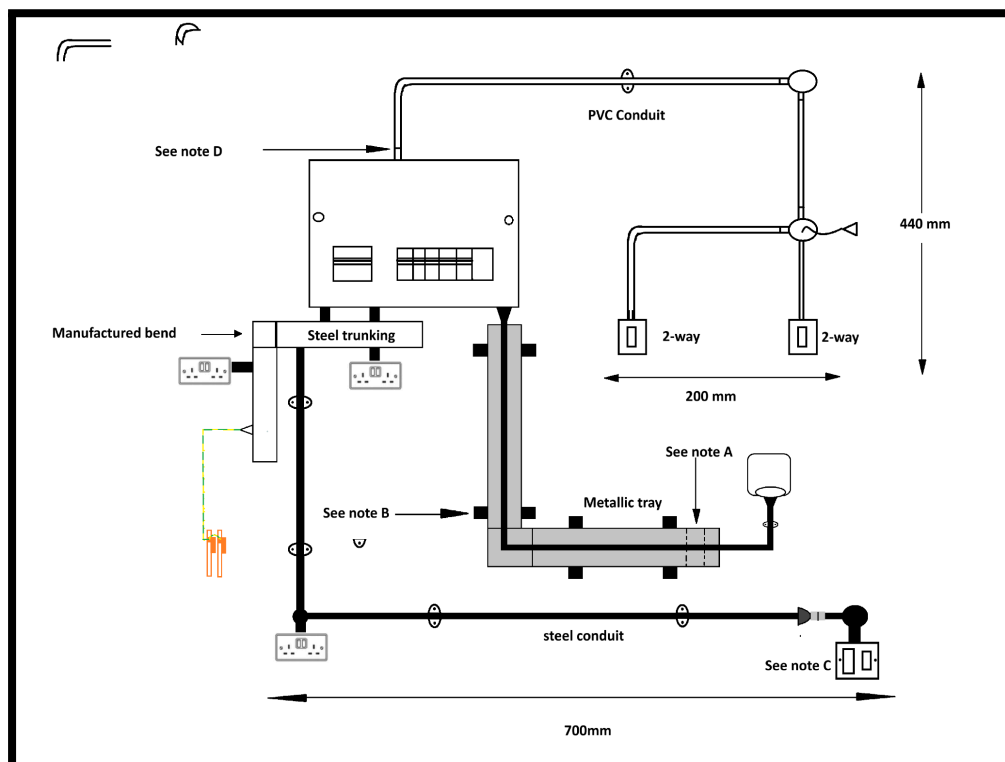


Overview of the practical exam for 2365	1
Light switch Step one	2
Light Switch Step Two	2
Light switch Step three	3
Steel conduit - Ring Circuit	3
SWA Radial Circuit	3

Overview of the practical exam for 2365


The overall schematic for the circuit board that I my cohorts and I had to installation as part of the final assessment for the 2365 level 2 diploma.




Light switch

The light circuit is on a 6 amp breaker.


Step One light

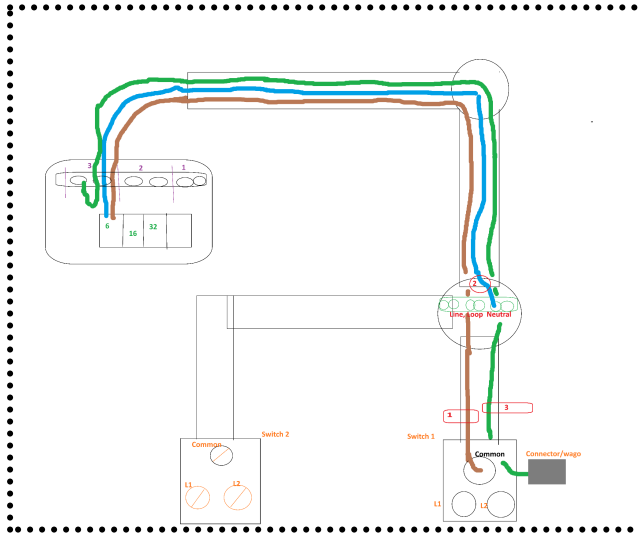


Step Two

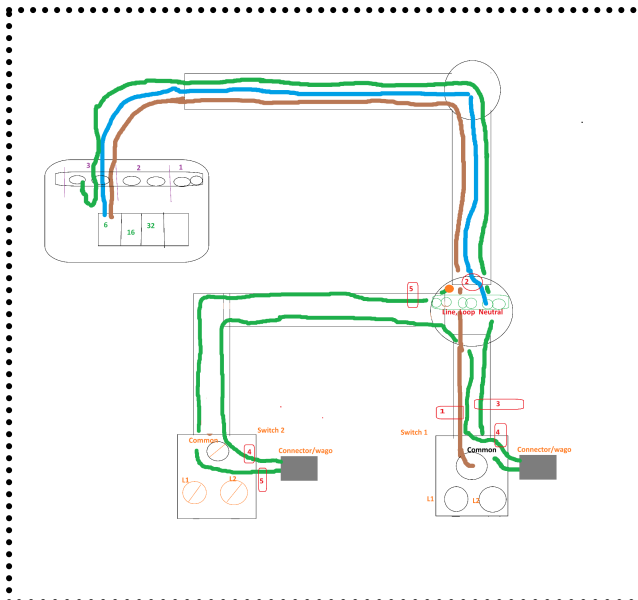

Step three - strappers

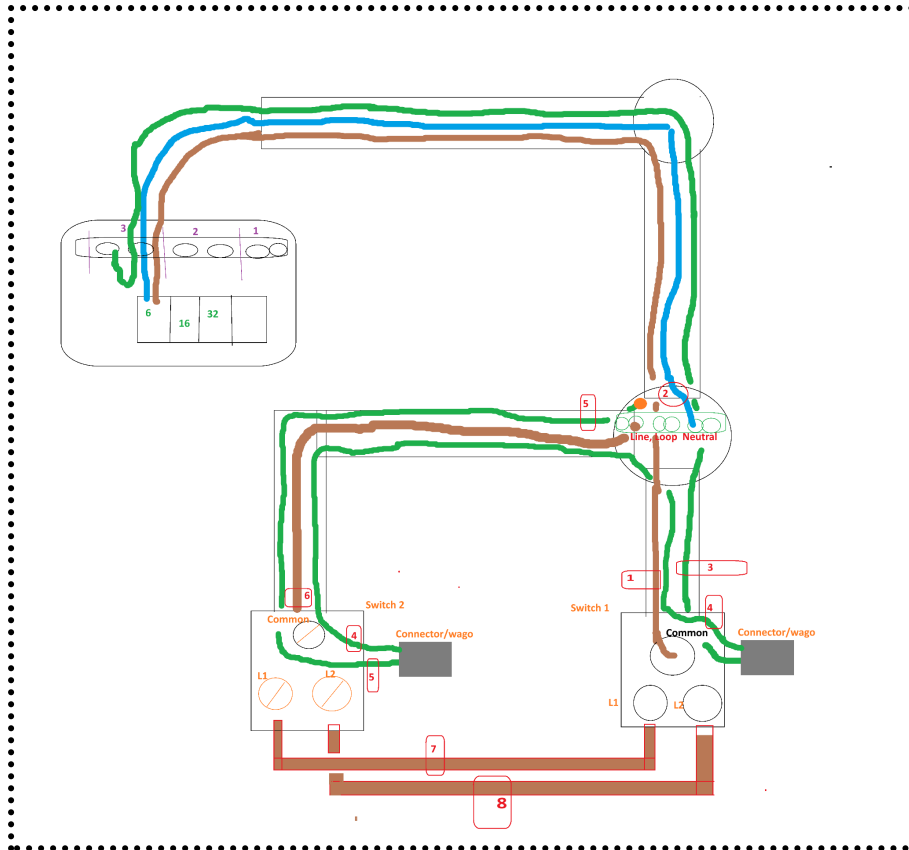

Step three - strappers

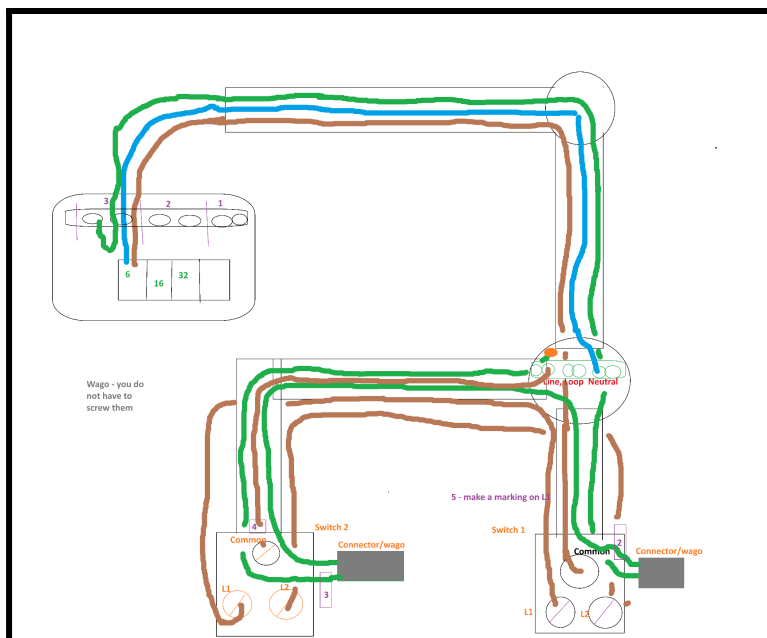

Steel conduit - Ring Circuit

Is on a 32 amp breaker.

The ring circuit as long as you have 2 blue 2 brown and 2 green at every point that means you will have the same at the fuse board both L and N both connected to the breaker and green to earth.

SWA Radial Circuit

The SWA radial circuit is on a 16 amp breaker.

The swa brown, black and grey in the fuse board black is earth. Grey is n. Don't forget sleeving. You will be fine.

Brown => Live

Black => **yellow/green** sleeving => earth

Grey => **Blue** sleeve => Neutral