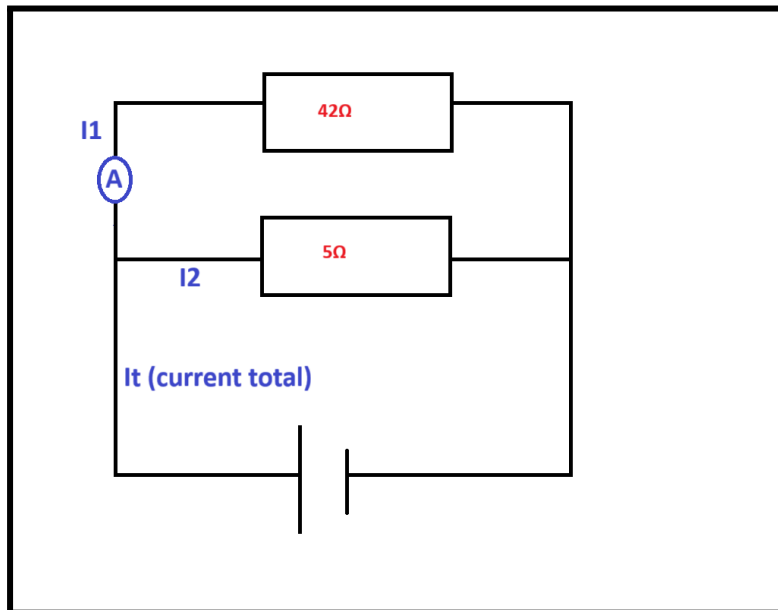


Lesson 19

Theory



Parallel circuit

- The **current** changes whereas the **voltage** is constant

The I_T = **Current Total**

The current can either flow down I_1 or the current can flow down I_2 .

Practical

