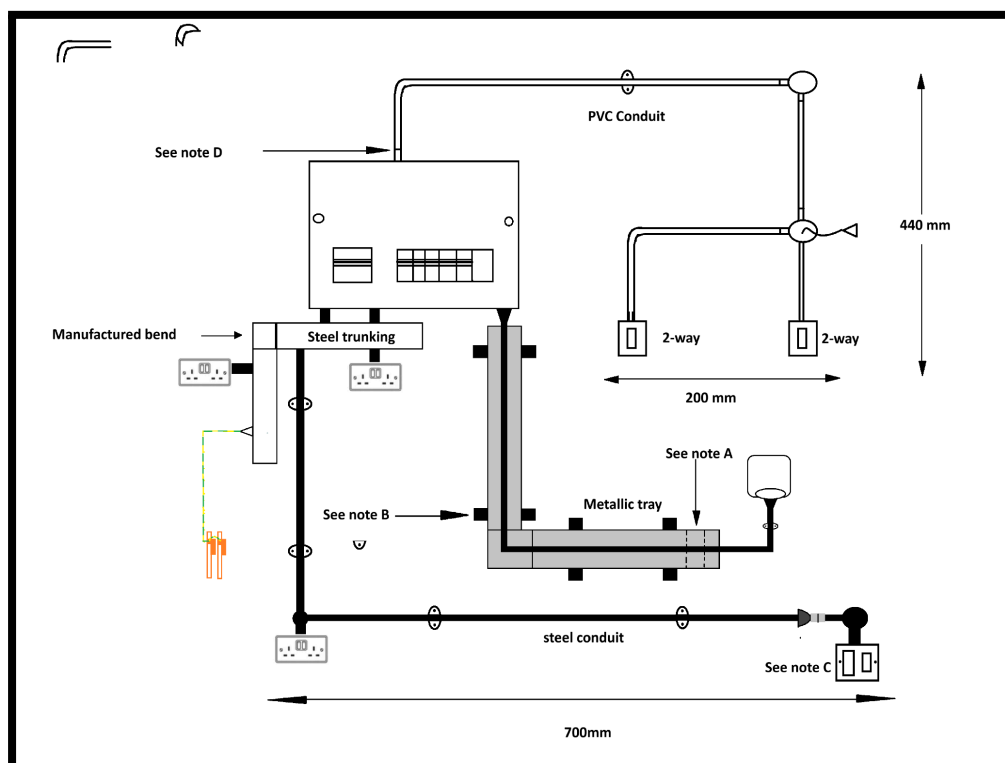



Overview of the practical exam for 2365.....	1
Light switch Step one.....	2
Light Switch Step Two.....	2
Light switch Step three.....	3
Steel conduit - Ring Circuit.....	3
SWA Radial Circuit.....	3

The overall schematic for the circuit board that I have to design.


Overview of the practical exam for 2365




Light switch Step one

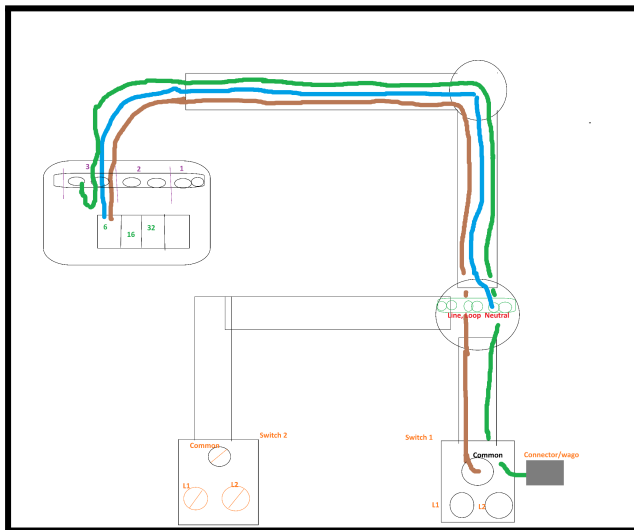

Light Switch Step Two

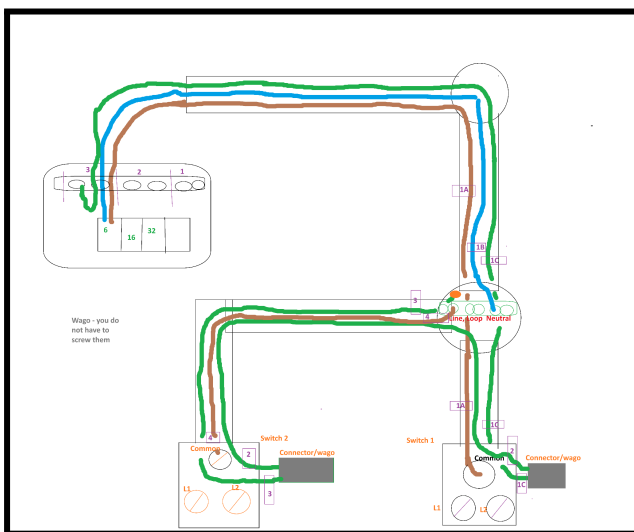

Light switch Step three

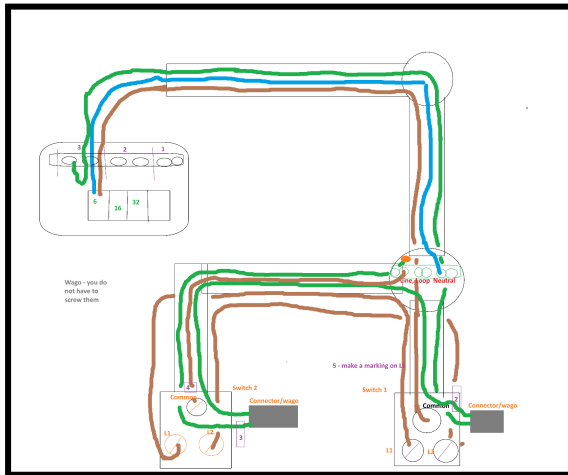

Steel conduit - Ring Circuit

The ring circuit as long as you have 2 blue 2 brown and 2 green at every point that means you will have the same at the fuse board both L and N both connected to the breaker and green to earth.

SWA Radial Circuit

The swa brown, black and grey in the fuse board black is earth. Grey is n. Don't forget sleeving. You will be fine.

Brown => Live

Black => **yellow/green** sleeving => earth

Grey => **Blue** sleeve => Neutral